

Ans: C

Q17

Total resistance of circuit

$$= 3.0 + (1/6 + 1/6)^{-1} = 6.0 \, \Omega$$

Total current in circuit = $12 / 6.0 = 2.0 \, \text{A}$

Current through Y = $2.0 / 2 = 1.0 \, \text{A}$

Ans: B

Q18