

Q18

Effective resistance across Y and voltmeter = $R / 2$

Potential difference across Y and voltmeter = $[(R/2) / (R + R/2)](6.0) = 2.0 \text{ V}$

Ans: B