
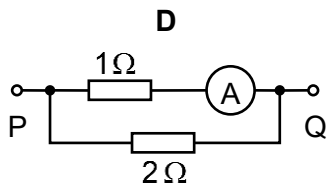
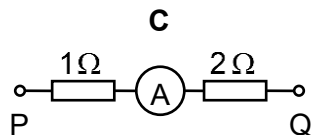
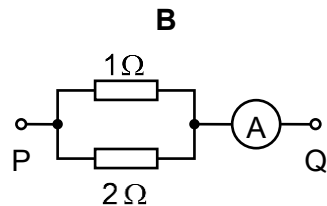


23 In each arrangement of resistors, the ammeter has a resistance of $3\ \Omega$.

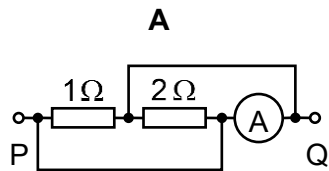Which arrangement gives the smallest reading on the ammeter when the same potential difference is applied between points P and Q?



24 A charged particle is projected with velocity v into an evacuated region. A uniform electric