

		$(8.5 \times 10^{-4} - 1.0 \times 10^{-4})$
23	C	The smallest reading on the ammeter means smallest current passing through it. Ammeter has a resistance of 3Ω. Option A: Incorrect. Current passing through ammeter, $I = \frac{V}{3}$, because ammeter is in parallel connection with the 1Ω and 2Ω resistors. Option B: Incorrect. Current passing through ammeter, $I = \frac{V}{3.67}$. Option C: Correct. Current passing through ammeter, $I = \frac{V}{6}$. Option D: Incorrect. Current passing through ammeter, $I = \frac{V}{4}$.
24	D	For zero deflection, magnetic force = electric force