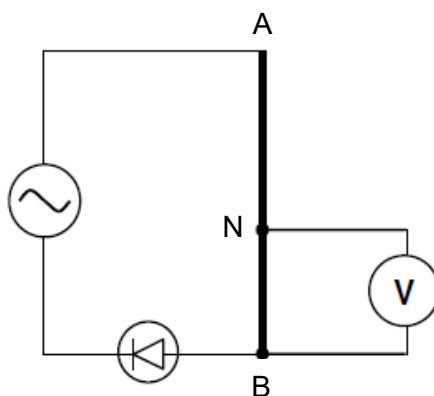


- 26** The uniform wire AB has length 1.0 m and resistance of $10\ \Omega$. It is connected in series with an a.c. supply and an ideal diode.



When NB is 40 cm, the a.c. voltmeter gives a steady reading of 2.5 V.

What is the instantaneous peak power provided by the supply?

- A** 0.63 W
- B** 3.9 W
- C** 7.8 W
- D** 16 W

27 Electrons are accelerated from rest through a potential difference V