

		B-field must be into the coil. Thus, induced current in the coil is clockwise.
26	D	The a.c. is half-wave rectified with a single diode.. Voltmeter reads the r.m.s. voltage, $V = 2.5 \text{ V}$ So peak voltage across NB = $2(2.5) = 5.0 \text{ V}$ By potential divider principle, $\frac{V_{AB}}{V_{NB}} = \frac{L_{AB}}{L_{NB}} = \frac{100}{40} \rightarrow V_{AB} = V_o = \left(\frac{100}{40}\right) V_{NB} = \left(\frac{100}{40}\right) (5.0) = 12.5 \text{ V}$ $\text{Peak power} = \frac{V_o^2}{R} = \frac{12.5^2}{10} = 15.6 = 16 \text{ W}$
27	B	h