

		$V_x = \frac{(2d)^2}{(2d)^2 + 4d^2} V$
22	A	As V increases, I/V ratio increases, V/I ratio decreases, R decreases.
23	B	Effective resistance of right portion increases. Using potential divider principle, S is