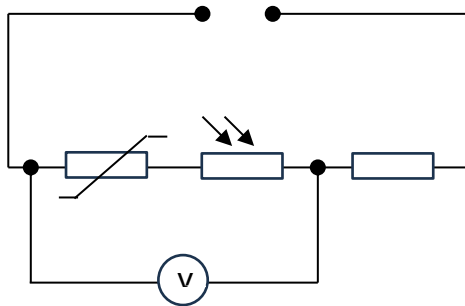


- 21** A negative temperature coefficient thermistor, an LDR and a fixed resistor are connected in series to a power supply. A voltmeter is placed across the thermistor-LDR combination.



Which conditions of brightness and temperature will produce the smallest reading on the voltmeter?

		temperature	brightness	
	A	high	high	
	B	high	low	

[Turn over

	C	low	high	
	D	low	low	
	Answer: A Smallest reading on the voltmeter, the total resistance of the thermistor and the LDR is the lowest. Lowest resistance of a NTC thermistor occurs when temperature is high Lowest resistance of LDR occurs when brightness is high			

22	A power supply and a solar cell are compared using the potentiometer circuit shown
-----------	--