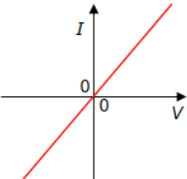
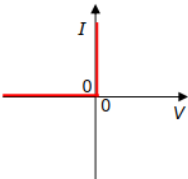
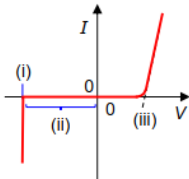


21

Answer: D

After overcoming the threshold voltage, the diode's resistance become negligible. The resistance of the fixed resistor is shown by having a constant V to I ratio, i.e. a straight line graph that cuts through the origin.

ohmic resistor	semiconductor diode	
a resistor in which the current flow is directly proportional to potential difference across it, if temperature and other physical conditions are kept constant	a component which allows current to flow in one direction from higher potential to lower potential <i>*more treatment in H218 Alternating Currents</i>	
	ideal diode	non-ideal diode
		

22

Answer: C