

24	Answer: A
	$V_{15\Omega} = V_R + V_{2.0\Omega} \text{ and using } V = IR$ $(0.48)(15) = (0.45)R + (0.45)(2.0)$ $R = 14 \Omega$ $V_{15\Omega} = E - V_r$ $(0.48)(15) = 10 - (0.45 + 0.48)r$ $r = 3.0 \Omega$

