

21	A	Resistance R is the ratio of V to I. To determine the change of R, analyse the ratio $\frac{I}{V}$ i.e. the gradient of the line from origin to the desired point on the graph. From W to X: $\frac{I}{V}$ is constant, thus the inverse of the ratio, R is constant. From X to Y: $\frac{I}{V}$ is increasing, thus the inverse of the ratio, R is decreasing. From Y to Z: $\frac{I}{V}$ is decreasing, thus the inverse of the ratio, R is increasing.
22	C	The readings of V_1 and V_2 are both zero.