

22	C	The readings of V_2 and V_3 are both zero. No current flows through the resistor that V_2 is connected across and the resistance of a diode is zero.
23	A	When the ammeter is zero