

21	D	At null point, $E_2 = \frac{3R}{3R + 2R + R} E_1$ Hence $\frac{E_1}{E_2} = 2.0$
22	B	The given circuit is similar to the circuit below.