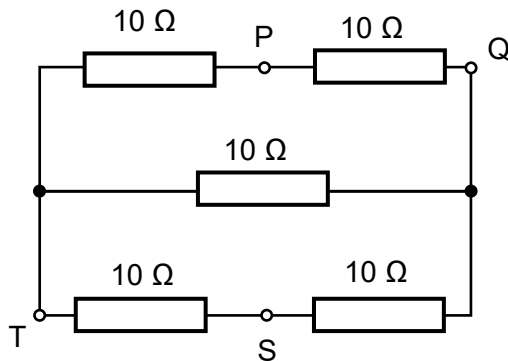


22

B

The given circuit is similar to the circuit below.



Thus, calculating the effective resistance across QT,

$$R_{QT} = \left(\frac{1}{10+10} + \frac{1}{10} + \frac{1}{10+10} \right)^{-1} = 5.0 \, \Omega$$

23

B

Along PQ and RS, magnetic flux density B varies inversely proportional to