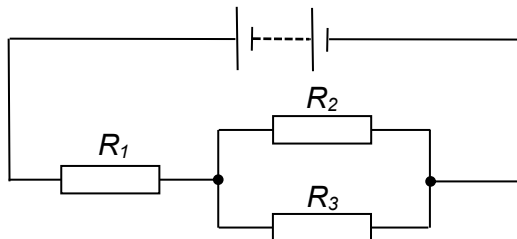


- 21 The diagram shows a network of three identical resistors connected to a battery of negligible internal resistance.



What is the ratio of $\frac{\text{power dissipated in } R_1}{\text{power dissipated in } R_2}$?

- A 1 B 2 C 4 D 9

Ans: C

$$\text{Total resistance of } R_2 \text{ and } R_3 = \left(\frac{1}{R} + \frac{1}{R} \right)^{-1} = \left(\frac{2}{R} \right)^{-1} = \frac{1}{2}R$$

$$I = \frac{E}{R_{\text{total}}} = \frac{E}{R + \frac{1}{2}R}$$

$$\text{p.d. across } R_1, V_1 = \frac{E}{R + \frac{1}{2}R} (R) = \frac{2}{3}E$$

$$\text{p.d. across } R_2, V_2 = E - \frac{2}{3}E = \frac{1}{3}E$$

$$\frac{P_1}{P_2} = \frac{\frac{V_1^2}{R}}{\frac{V_2^2}{R}} = \frac{2^2}{1^2} = 4$$

22 A typical potentiometer circuit is shown