

28	A	The average power of R without diode = $I_{rms}^2 R = 0.50 I_o^2 R$ When the diode is connected in the circuit, the average power of R will be halved ($0.25 I_o^2 R$) since it only received power for half the period.
29	D	Derive using wave particle duality and KE