

20 Ans: A

Resistance, $R = \frac{\rho l}{A}$ and potential drop across each wire $V = IR = I \left(\frac{\rho l}{A} \right) = I \rho \left(\frac{l}{A} \right)$

Since current and resistivity are constants, the potential drop increases with distance from X (i.e. length of wire in this case), and the smaller the cross-sectional area A , the larger is the drop per unit length of wire. So the last segment has the largest potential drop per unit length.

21 Ans: A