

26 **Ans: B**

$$V_p I_p = V_s I_s$$

$$I_s = \frac{120 \times 60}{4500} = 1.6A$$

$$\text{Percentage power lost} = \frac{I_s^2 R}{P_{total}} = \frac{1.6^2 \times 1.0}{120 \times 60} \times 100\% = 0.036\%$$

26

27 Ans: D