

- 5 (a) current (through a conductor is directly) proportional to potential difference (across the conductor) or vice versa
(provided that) temperature (of conductor remains) constant [1]
- (b) (i) $R = \rho L / A$
 $\rho = (18 \times 7.2 \times 10^{-8}) / 0.94 = 1.4 \times 10^{-6} \Omega \text{ m}$ [1]
- (ii) current in the battery: increase [1]
 voltmeter reading: decrease [1]
- (iii) cross marked on the resistance wire to right of the arrowhead of S, but not touching the right-hand end of the resistance wire [1]
- (c) (i) $I = Anvq$
 $q = 0.93 / [(7.2 \times 10^{-8}) \times (9.0 \times 10^{28}) \times (1.3 \times 10^{-3})]$
 $q = 1.1 \times 10^{-19} \text{ C}$ [1]
- (ii) charge / q (value) is below $1.6 \times 10^{-19} \text{ (C)}$ [1]
or
 charge cannot be below $1.6 \times 10^{-19} \text{ (C)}$
or
 (the charge carriers / q) should have a charge of $1.6 \times 10^{-19} \text{ (C)}$
- (d) Before t_1 / when current constant, the (total) resistance is constant
- At t_1 / when current increases, the (total) resistance decreases (due to decrease of external resistance)
- After t_1 , temperature (of lamp) increases so the resistance of the lamp increases (so total resistance increases so the current in the ammeter decreases)

[3]

