

$$\Rightarrow F_Y > F_X$$

20 D Break in +ve wire of cable $\Rightarrow$ voltmeter reading = 0 when connected to X or Y

Break in connection within motor $\Rightarrow$ voltmeter reading = 24 V when connected to X and 0 V when connected to Y

Break in -ve wire of cable $\Rightarrow$ voltmeter reading = 24 V when connected to X or Y

21 A In dark condition: