

a larger angle

5 **(ai)** $V_{\text{rms}} = \frac{V_0}{\sqrt{2}} = \frac{170}{\sqrt{2}} = 120 \text{ V}$

A1

(aii) $\omega = 2\pi/T = 314$
 $T = 0.0200 \text{ s}$

A1

(b) **(i)** $\frac{V_S}{V_P} = \frac{N_S}{N_P}$
 $\frac{V_S}{170} = \frac{3500}{2000}$
 $V_S = 298 \text{ V}$

C1

A1

(ii)

$$\begin{aligned} V_S &= I_S R \\ 298 &= I_S (130) \\ I_S &= 2.288 \text{ A} \\ \frac{I_P}{I_S} &= \frac{N_S}{N_P} = \frac{3500}{2000} \\ I_P &= 4.00 \text{ A} \end{aligned}$$

C1

A1

b

iii

$$\begin{aligned} V_S &= I_S R \\ 298 &= I_S (130) \\ I_S &= 2.288 \text{ A} \\ \frac{I_P}{I_S} &= \frac{N_S}{N_P} = \frac{3500}{2000} \\ I_P &= 4.00 \text{ A} \end{aligned}$$

C1

Power loss due to
Induced Eddy currents
Hysteresis los
Any possible causes

A1

B1

(c)

