

- 4 (a) $\frac{R}{0.75 + R + 5.5} \times 4.0 = 1.3$ C1
 $R = 3.0 \Omega$
- p.d. across AB = $\frac{5.5}{0.75 + 3.0 + 5.5} \times 4.0$ C1
 $= 2.4 \text{ V}$ A0
- (b)(i) $E = \frac{1.50 - 0.56}{1.50} \times 2.4$ C1
 $= 1.5 \text{ V}$ A1
- (b)(ii) As C is shifted closer to A, the potential at C increases, thus increasing the potential difference between BC. M1
 Since the potential between BC will become larger than the terminal p.d. of cell Q, current will now flow from C to B through cell Q. A1
- (c)(i) $\frac{R}{L} = 5.5 / 150 = 0.0367 \Omega \text{ cm}^{-1}$ C1
 $R = 2 \times 15 \times 0.0367 + \frac{1}{5} \left(\frac{150 - 2 \times 15}{5} \times 0.0367 \right)$ C1
 $= 1.28 \Omega$
 $= 1.3 \Omega$ A0
- (c)(ii) Since $I = n A v q$, number density n , cross-sectional area A and charge q are the same in both sections XY (consider a single wire) and AX, $v \propto I$. C1
 the current through a single wire in XY is 1/5 of the current through AX.
 OR
 Since the same current flows through sections AX and XY (consider XY as a whole), $v \propto 1/A$.
 the cross-sectional area of XY is 5 times the cross-sectional area of AX.
 drift velocity v is greater in AX than in XY A1