

Q20 Ans: B

For the voltmeter reading to be highest, the combined resistance of the thermistor and LDR has to be lowest (by potential divider principle).

High brightness (i.e. high intensity of light) would give LDR lowest resistance. High temperature would give thermistor lowest resistance.

Q21 Ans: C