

Q26 Ans: B

Current from the a.c. supply can flow in both directions around the circuit.
But the setup of diodes result in current flowing through R to be only in the upward direction.

Q27 Ans: B