
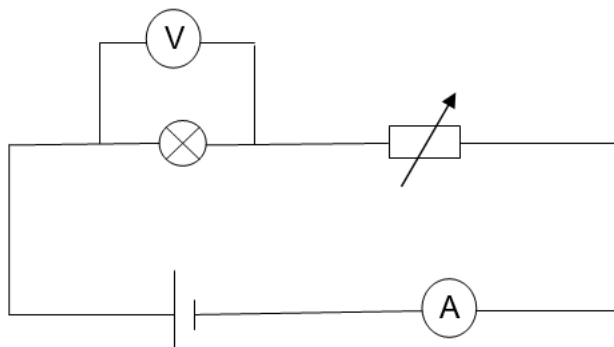


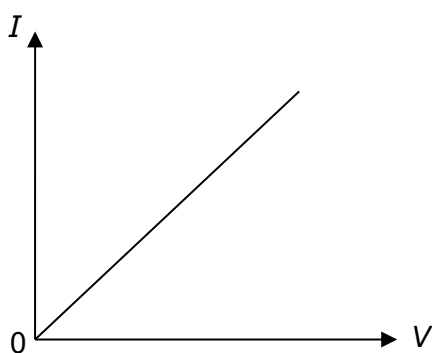22 In the circuit shown below, the current can be varied by means of the rheostat.




Which one of the following graphs best shows how the ammeter reading I varies with the voltmeter reading V ?


A




B

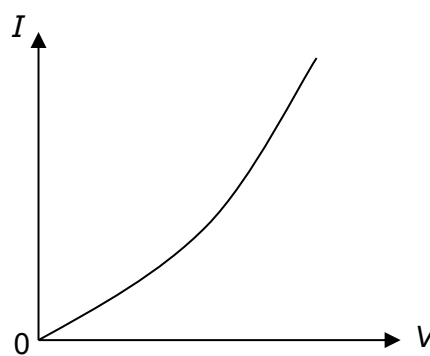

C

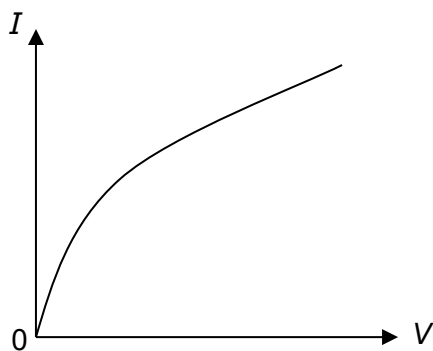

D

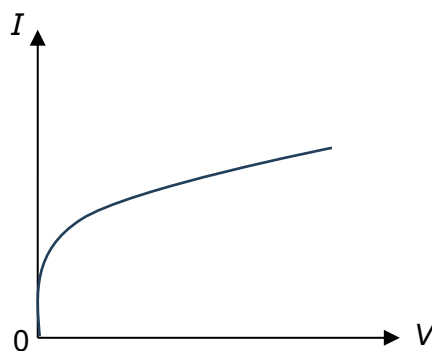

Ans: C

The resistance of the bulb increases with the temperature. Also, it is never zero (that's why D is wrong).

