

21 A by potential divider rule:

$$\frac{R_1}{R_1 + R_2} E_{\text{sec}} = \frac{60}{L} E_{\text{main}} \quad \text{——— (1)}$$

$$\frac{R_2}{R_1 + R_2} E_{\text{sec}} = \frac{20}{L} E_{\text{main}} \quad \text{——— (2)}$$

$$\frac{(2)}{(1)} : \frac{R_2}{R_2} = \frac{20}{60} = \frac{1}{3}$$

22 B with resistor across A and B, there is complete circuit for which induced current can flow, as