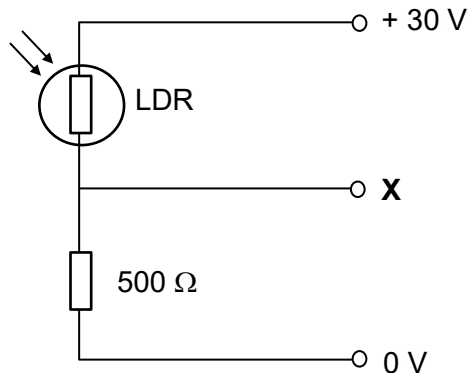


24. The light dependent resistor (LDR) and a $500\ \Omega$ resistor form a potential divider between voltage lines held at $+30\text{ V}$ and 0 V as shown.



The resistance of the LDR is $1000\ \Omega$ in the dark but drops to $100\ \Omega$ in bright light.

What is the corresponding change in the potential at **X**?

- A** A rise of 25 V
- B** A rise of 15 V
- C** A fall of 15 V
- D** A fall of 25 V