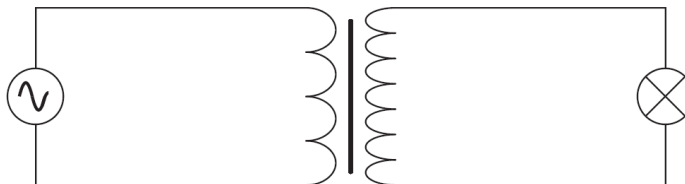


27. The primary coil of a step-up ideal transformer is connected to a source of alternating potential difference. The secondary coil is connected to a lamp.



Which line, **A** to **D**, in the table correctly describes the flux linkage and current through the secondary coil in relation to the primary coil?

	$\frac{\text{secondary magnetic flux linkage}}{\text{primary magnetic flux linkage}}$	$\frac{\text{secondary current}}{\text{primary current}}$
A	> 1	< 1
B	< 1	< 1
C	> 1	> 1
D	< 1	> 1