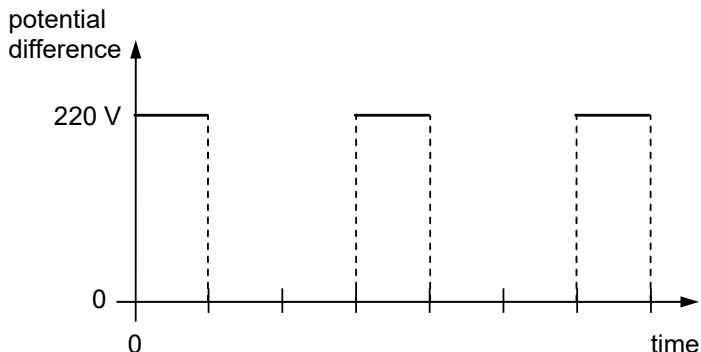


28. An alternating current is supplied to a rectifier. The output from the rectifier has the shape shown in the diagram, with a maximum value of 220 V.



This output is used as the supply to a resistor of resistance $60.0 \, \Omega$.

What are the r.m.s. values of the current and the power to the resistor?

	r.m.s. current / A	power / W
A	1.22	89.6
B	1.83	202
C	2.12	269
D	2.59	403