

		Option D. Electric field strength at a point is the electric force acting on a charge per unit positive charge placed at that point.
21	A	At $I = 0.1 \text{ A}$, V across resistor (1.0V) and V across thermistor (2.0) adds up to be the e.m.f of the battery. If resistor is doubled, with same current, voltage across resistor $= 0.1 \times (2 \times 10) = 2 \text{ V}$. Hence e.m.f of new battery $= 2 + 2 = 4 \text{ V}$
22	A	Option A is false as no current passes through the lower circuit at balance point, hence the internal resistance of cell B does not affect the p.d. across the lower circuit