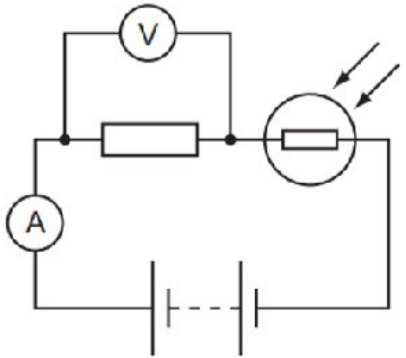
24 A potential divider circuit with a light-dependent resistor (LDR) is shown below.



The intensity of the light incident on the LDR is reduced.

Which row correctly describes the observed change on the ammeter and voltmeter readings?

	Ammeter reading	**Voltmeter reading**
A	decreases	decreases
B	decreases	increases
C	increases	stays the same
D	stays the same	decreases