21 When three identical capacitors of capacitance C are connected to a cell in series, the total charge stored is Q_1. When the same capacitors are connected to the same cell in parallel, the total charge stored is Q_2.

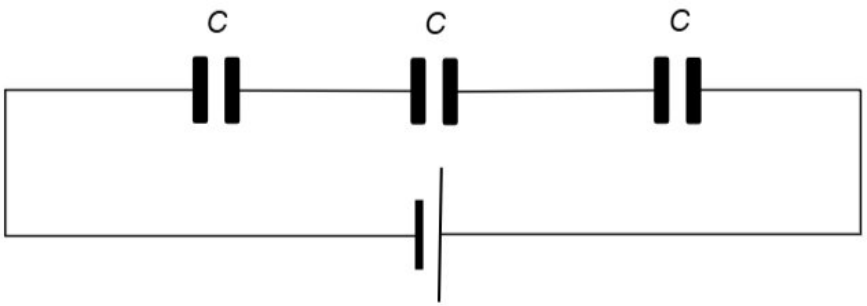

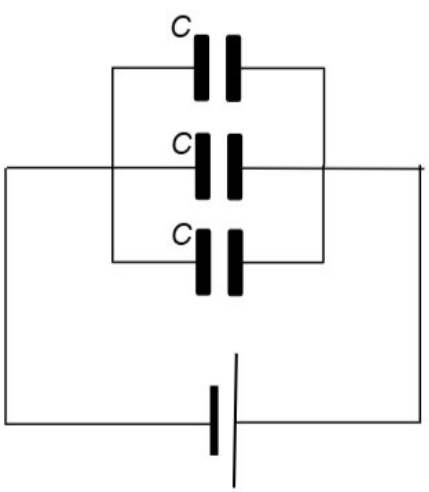

What is the ratio $\frac{Q_1}{Q_2}$?

A $\frac{1}{9}$ **B** $\frac{1}{3}$ **C** 3 **D** 9