22 A constant voltage DC source is connected across three identical resistors Q, R and S, of resistance 50 Ω.

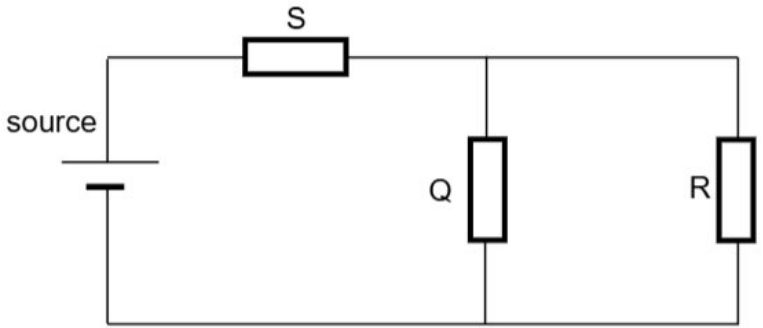

If the source is supplying a total power of 12 W, what is the power dissipated in resistor R?

A 2.0 W **B** 3.0 W **C** 4.0 W **D** 8.0 W