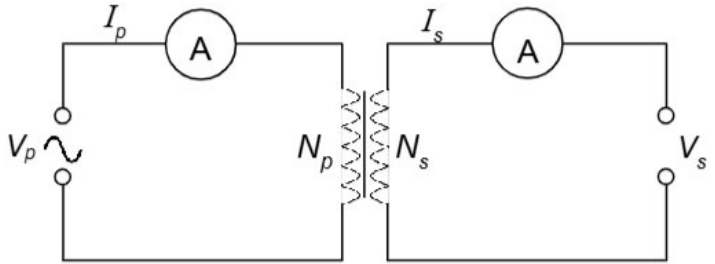
27 The following circuit was set up to test a transformer. The input a.c. voltage V_p is 450 V, with a current I_p of 4.0 mA. The number of turns in the secondary coil, N_s is 240 with a current I_s of 120 mA.



The transformer was 100% efficient.

What is the number of turns in the primary coil, N_p and output a.c. voltage, V_s?

	N_p	V_s
A	8	13500
B	8	15
C	7200	13500
D	7200	15