		Total charge = 6480 + 1080 = 7.6×10^3 C
22	**D**	For the resistance to be constant, the graph must be a straight line that passes through the origin. Resistance is the ratio of V/I.
23	**D**	The effective resistance of the 3 resistors in parallel is $\frac{R}{3}$.