18	**B** Potential difference across the resistance R is given as $V = IR$. Hence, $IR = E - Ir$ From the data, we form two equations: $3.0 = E - 1.0\,r$ … (1) $4.8 = E - 0.4\,r$ … (2) Solving the equations simultaneously, $r = 3.0\ \Omega$ and $E = 6.0$ V
19	**A**