24	**Answer: A**
	The resistor and thermistor are connected in series. Therefore, the current flowing through them are the same. The total p.d. across both components must add up to 12 V and only option A satisfies that. p.d. across resistor = 5.4 V p.d. across thermistor = 6.6 V p.d. across both resistor and thermistor = 5.4 + 6.6 = 12 V