		$Ah = A\,(N/V) = A\,(N/Al) = N/l$
21	**D**	A and B are wrong because the diode is connected in reverse-bias. When temperature of the thermistor is low, resistance is high and hence p.d. across the thermistor is high. The heater should be connected across the thermistor.
22	**C**	From I = Q / t = 6.0 / (2 × 60) = 0.050 A