		thermistor is right. The heater should be connected across the thermistor.
22	**C**	From I = Q / t = 6.0 / (2 × 60) = 0.050 A From P = V I $\frac{48}{2\times60}$ = V (0.050) V = 8.0 V Thus, from E = IR + Ir 9.0 = 8.0 + (0.050) r r = 20 Ω
23	**D**	For circular motion inside a uniform magnetic field,