23	**C**	Capacitance for each parallel network = $C + C + C = 3C$ Total capacitance = $(1 / 3C + 1 / 3C)^{-1} = 3C / 2$
24	**B**	P and Q have the same speed (pass through velocity selector undeviated).