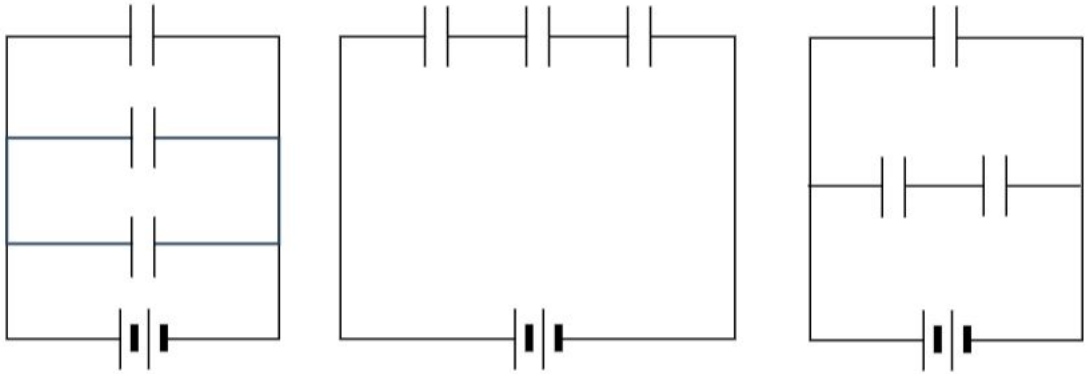
23 Three identical capacitors are connected to a battery in three different arrangements as shown below.



Which of the following lists the arrangements in order of increasing capacitance?

A PRQ **B** QRP **C** PQR **D** RQP

Ans: **B**

P: $C_{eff} = 3C$

Q: $\frac{1}{C_{eff}} = \frac{3}{C}$

R: $C_{eff} = C + \frac{1}{2/C}$