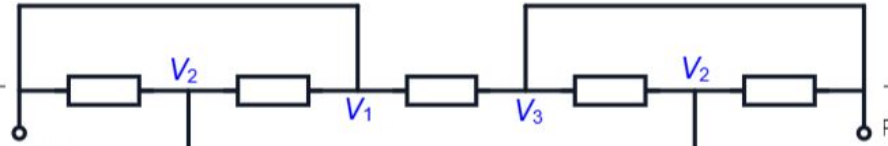
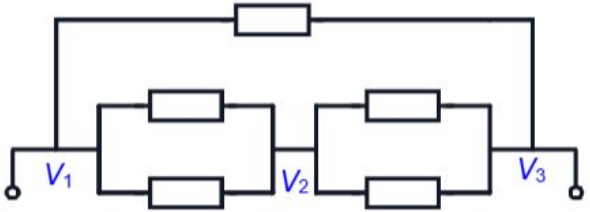
		Hence, $\frac{\text{peak current of square wave}}{\text{peak current of half wave rectified sinusoidal wave}} = \frac{1}{2}$
22	**A**	Assume A has a high potential and B has low potential. Let's label V_1, V_2, V_3, etc for points of potential where V_1 is the highest. Remember that potential remains the same along a wire. 

		Redrawing the circuit,  Hence, effective resistance = ½ R = 0.50 Ω
23	**D**	Since the currents are in opposite directions, the magnetic fields between the wires are in the same direction, so they cannot cancel there. Hence the zero-