Decrease = $V_X/I_X - V_Y/I_Y$

22 **Ans: A** (2014 P1 Q29)

By potential divider principle, pd across each 800 Ω resistor = 800/ (800+800) X 12 V
= 6 V

Let the bottom wire of the circuit be at zero V (earth potential).
→ pot at Y = +6 V.
Similarly, we deduce potential at pt X = +6 V too.
Thus, pd across XY, i.e. pd across the wire = 0.
Hence by V = IR, current betw X & Y = 0.