23 Four identical resistors are connected in a circuit as shown to a battery of negligible internal resistance.

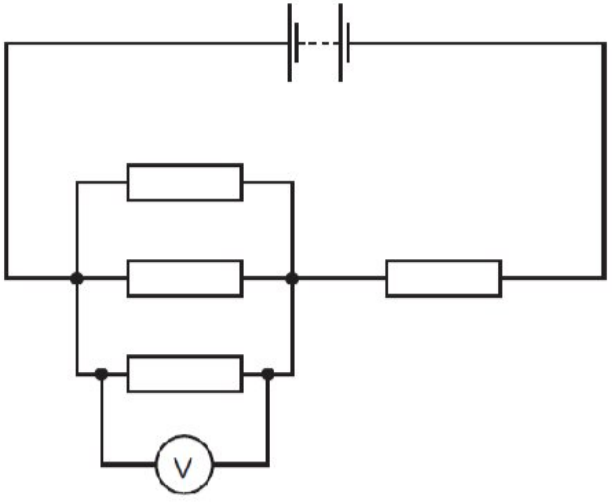

The voltmeter reads 3.0 V.

What is the e.m.f. of the battery?

A 3.0 V **B** 4.0 V **C** 6.0 V **D** 12.0 V