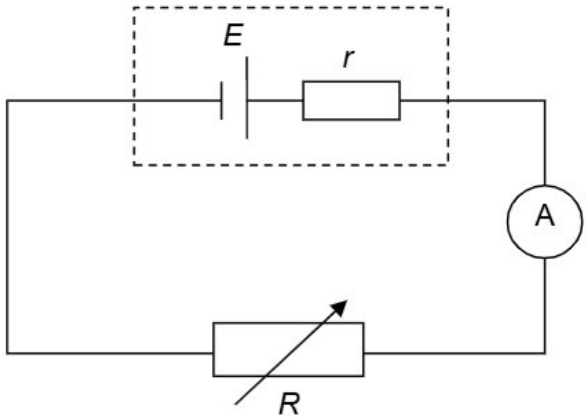
18 A battery of e.m.f. E and internal resistance r delivers a current I through a variable resistance R.



R is set at two different values and the corresponding currents I are measured using an ammeter of negligible resistance.

R / Ω	I / A
3.0	1.00
12.0	0.40

What is the value of the internal resistance r?

A 1.3 Ω **B** 3.0 Ω **C** 6.0 Ω **D** 13 Ω