19 Four identical capacitors are connected to a cell as shown.

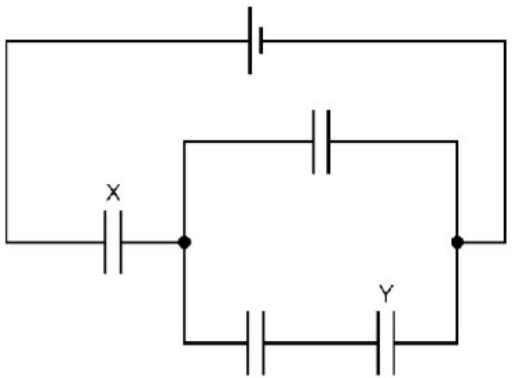

The charge stored on capacitor X is 6 μC.

What is the charge stored on capacitor Y?

A 2 μC **B** 3 μC **C** 4 μC **D** 6 μC