26 An alternating current with a rectangular waveform as shown below flows through an 11 Ω resistor.

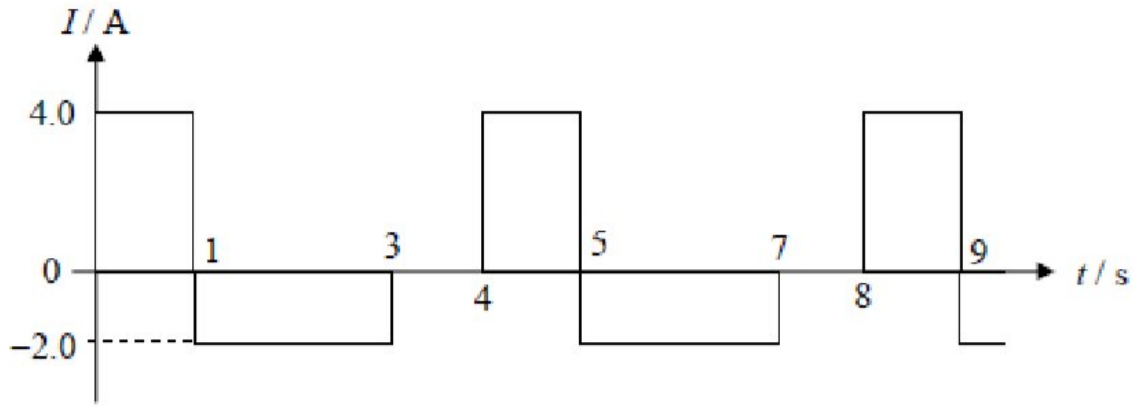

What is the average power dissipated by the resistor?

A 0 **B** 44 W **C** 66 W **D** 88 W