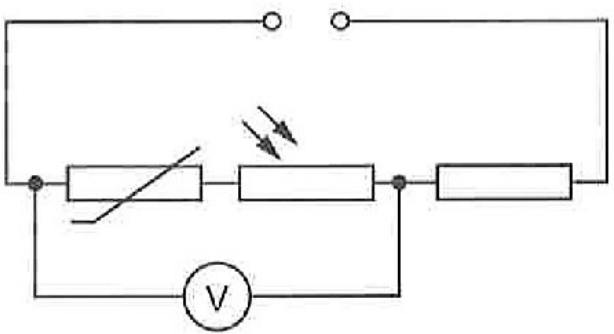
22 A negative temperature coefficient (NTC) thermistor, a light-dependent resistor (LDR) and a fixed resistor are connected in series to a power supply. A voltmeter is placed across the NTC-LDR combination.



What conditions of brightness and temperature will produce the largest reading on the voltmeter?

	temperature	brightness
A	high	high
B	high	low
C	low	high
D	low	low