23 The diagram shows a network of capacitors connected to a 12 V battery of negligible internal resistance.

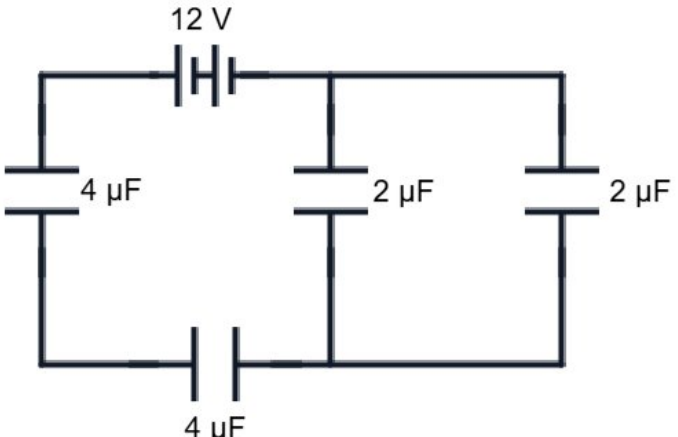

What is the total amount of charge circulated by the 12 V battery?

A 16 μC **B** 24 μC **C** 36 μC **D** 110 μC