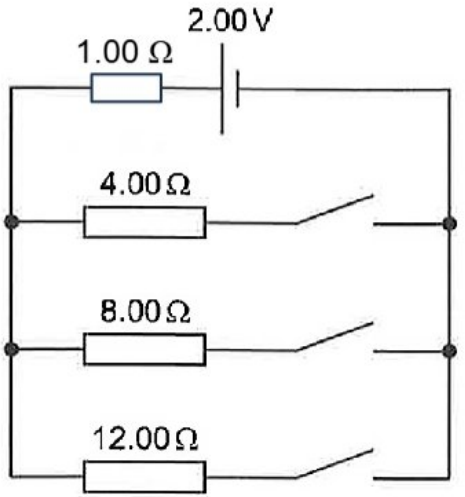
19 A cell of e.m.f. 2.00 V and internal resistance 1.00 Ω is connected to three resistors of 4.00 Ω, 8.00 Ω and 12.00 Ω as shown in the circuit diagram.



What is the current through the cell when every switch is closed?

A 0.0800 A **B** 0.500 A **C** 0.629 A **D** 0.917 A